

$$u = \hat{u} \cos(\omega t + \varphi)$$

\hat{u} ... Amplitude

$U_{pp} \dots 2\hat{u}$

φ ... Nullphasenwinkel

$t_n = \frac{\varphi}{\omega}$... Nullphasenzeit

$\varphi = 0$ Nullphase
 $\varphi_1 > \varphi_2 \rightarrow u_1$ eilt u_2 voraus
 $\varphi_1 - \varphi_2 \rightarrow$ Phasenverschiebung

$$\bar{u} = \frac{1}{T} \int_0^T u \, dt = 0$$

$$U = \sqrt{\frac{1}{T} \int_0^T u^2 \, dt} = \frac{\hat{u}}{\sqrt{2}}$$

$$|\bar{u}| = \frac{1}{T} \int_0^T |u| \, dt = \frac{2}{\pi} \hat{u}$$

für sinusförmige Funktionen



Effektivwert Sinusfunktion

ÜBERLAGERUNG SIN-FUNKTIONEN

$\omega_1 = \omega_2 \rightarrow u_3 = u_1 + u_2$ wieder sinusförmig

$\omega_1 \neq \omega_2 \rightarrow u_3$ nicht sinusförmig

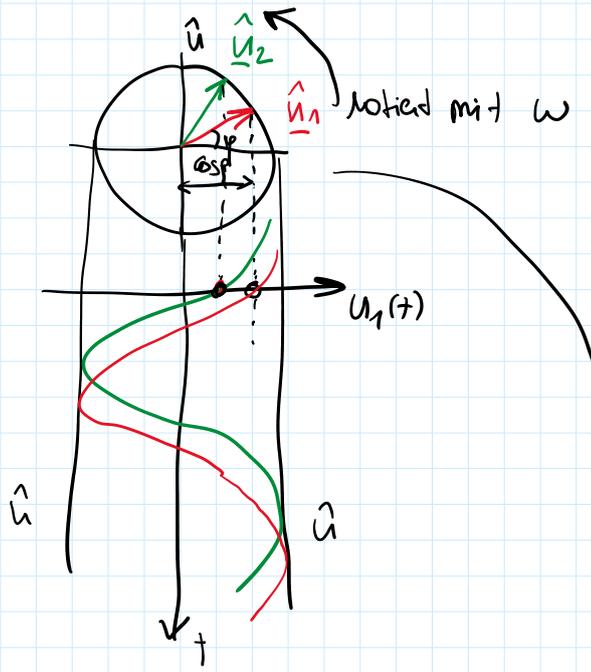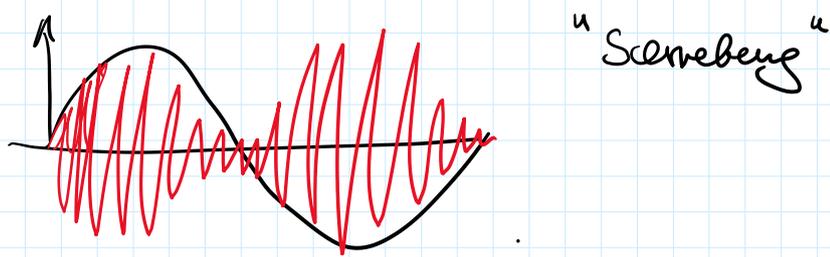$\omega_1 \approx \omega_2 \quad \omega = \frac{\omega_1 + \omega_2}{2} \quad \Delta\omega = \frac{\omega_1 - \omega_2}{2}$



$\text{Re}\{\hat{u}_1\} = \hat{u} \cdot \cos\varphi$
 $\text{Im}\{\hat{u}_1\} = \hat{u} \cdot \sin\varphi$
 $\hat{u}_1 = \sqrt{\text{Re}\{\hat{u}_1\}^2 + \text{Im}\{\hat{u}_1\}^2}$
 $\varphi = \arctan \frac{\text{Im}\{\hat{u}_1\}}{\text{Re}\{\hat{u}_1\}}$

$u(t) = \hat{u} \cos(\omega t + \varphi) + j \hat{u} \sin(\omega t + \varphi) = *$

$e^{j\varphi} = \cos\varphi + j \sin\varphi$ Eulersche Formel

$* = \hat{u} e^{j(\omega t + \varphi)} = \hat{u} e^{j\omega t} e^{j\varphi}$


$\hat{u} = \hat{u} e^{j\varphi} = \hat{u} \underline{\varphi}$

$\underline{u} = u e^{j\varphi} = u \underline{\varphi} \quad i^2 = -1 \quad i = \sqrt{-1}$

$$\underline{u} = u e - u \square$$

E 33 Summe zweier Ströme

$$\begin{aligned} \underline{I}_1 &= 1,5 \text{ A } \angle 0^\circ & i_1 &= \sqrt{2} \cdot 1,5 \text{ A } e^{j(\omega t + 0^\circ)} \\ \underline{I}_2 &= 0,5 \text{ A } \angle 120^\circ & i_2 &= \sqrt{2} \cdot 0,5 \text{ A } e^{j(\omega t + 120^\circ)} \\ \underline{I}_1 &= 1,5 \text{ A} + j0 \text{ A} \\ \underline{I}_2 &= -0,25 \text{ A} + j0,433 \text{ A} \\ \underline{I}_3 &= \underline{I}_1 + \underline{I}_2 = 1,25 \text{ A} + j0,433 \text{ A} \\ &= 1,32 \text{ A } \angle 19,1^\circ \end{aligned}$$

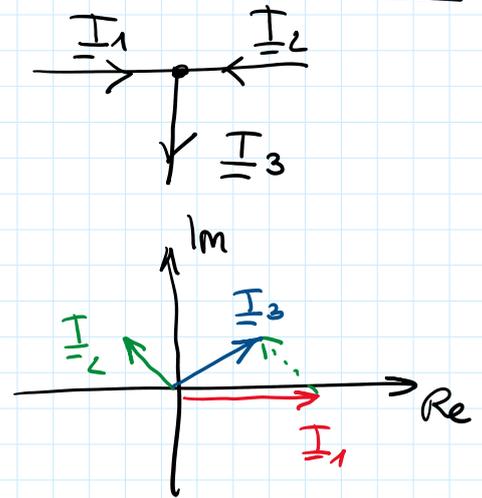


Kondensator | KAPAZITÄT

$$C = \frac{Q}{u} \quad [C] = 1 \text{ F}$$

$$dQ = C du$$

$$i = \frac{dQ}{dt} = C \frac{du}{dt}$$

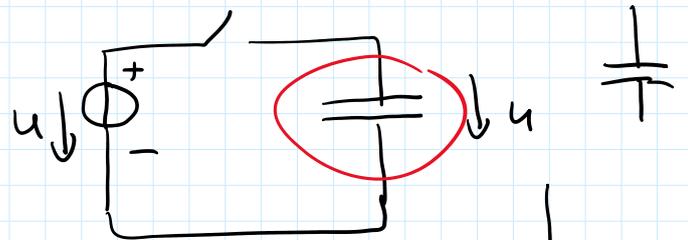


Reihe

$$\frac{1}{C_{ges}} = \frac{1}{C_1} + \dots + \frac{1}{C_n}$$

||


$$C_{ges} = C_1 + C_2 + \dots + C_n$$

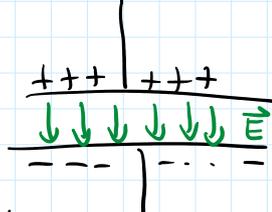

Spule | INDUKTIVITÄT

$$[L] = 1 \text{ H}$$

$$u = L \frac{di}{dt}$$

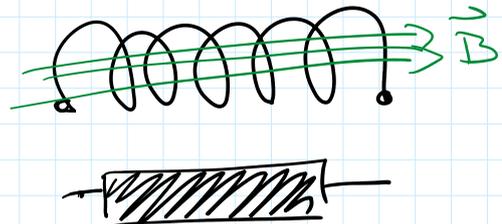

Reihe / Serie

$$L_{ges} = L_1 + \dots + L_n$$

||

$$\frac{1}{L_{ges}} = \frac{1}{L_1} + \dots + \frac{1}{L_n}$$

$$\underline{Y} = \frac{1}{\underline{Z}} = \frac{1}{z} \underline{L-p} = 5,21 \text{ mS } \underline{+15^\circ}$$



$$u(t) = 230 \text{ V} \cdot \sqrt{2} \cdot \cos(\omega t)$$

$$f = 50 \text{ Hz}$$
$$T = 4 \text{ ms}$$

$$\omega t = 2\pi \cdot 50 \cdot 4 \text{ ms}$$

Radiant!